

Digital Logic Design: a rigorous approach ©

Chapter 14: Shifters

part 1 - shifters

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

May 13, 2020

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>


Preliminary questions:

- 1 Which types of shifts are you familiar with in your favorite programming language? What are the differences between these shifts? Why do we need different types of shifts?
- 2 How are these shifts executed in a microprocessor?
- 3 Should shifters be considered to be combinational circuits? After all, they simply “move bits around” and do not compute “new bits”.

C/python: $A \ll 5$ $A \gg 5$

 Example

- assume that we place the bits of $a[1 : 12]$ on a wheel.
- $a[1]$ is at one o'clock, $a[2]$ is at two o'clock, etc.
- rotate the wheel, and read the bits in clockwise order starting from one o'clock and ending at twelve o'clock.
- the resulting string is a cyclic shift of $a[1 : 12]$.



Definition of a Cyclic Shifter

We denote $(a \bmod b)$ by $\text{mod}(a, b)$.


Definition

The string $b[n - 1 : 0]$ is a **cyclic left shift by i positions** of the string $a[n - 1 : 0]$ if

$$\forall j : b[j] = a[\text{mod}(j - i, n)].$$

 Example

Let $a[3 : 0] = 0010$. A cyclic left shift by one position of \vec{a} is the string 0100. A cyclic left shift by 3 positions of \vec{a} is the string 0001.



Definition of BARREL-SHIFTER(n)

Definition

A BARREL-SHIFTER(n) is a combinational circuit defined as follows:

Input: $x[n-1:0] \in \{0,1\}^n$ and $sa[k-1:0] \in \{0,1\}^k$
where $k = \lceil \log_2 n \rceil$.

Output: $y[n-1:0] \in \{0,1\}^n$.

Functionality: \vec{y} is a cyclic left shift of \vec{x} by $\langle \vec{sa} \rangle$ positions.
Formally,

$$\forall j \in [n-1:0] : y[j] = x[\text{mod}(j - \langle \vec{sa} \rangle, n)].$$

We often refer to the input \vec{x} as the **data input** and to the input \vec{sa} as the **shift amount input**. **To simplify the discussion, we assume that n is a power of 2, namely, $n = 2^k$.**

BARREL-SHIFTER(n) Implementation

We break the task of designing a barrel shifter into smaller sub-tasks of shifting by powers of two. We define this sub-task formally as follows.

A $\text{CLS}(n, 2^i)$ is a combinational circuit that implements a cyclic left shift by zero or 2^i positions depending on the value of its select input.

Definition

A $\text{CLS}(n, i)$ is a combinational circuit defined as follows:

Input: $x[n-1:0]$ and $s \in \{0, 1\}$.

Output: $y[n-1:0]$.

Functionality:

$$\forall j \in [n-1:0] : y[j] = x[\text{mod}(j - s \cdot i, n)].$$

$$y[j] = \begin{cases} x[j] & \text{if } s=0 \\ x[\text{mod}(j-i, n)] & \text{if } s=1 \end{cases}$$

Subtask: $\text{CLS}(n, i)$ Implementation

A $\text{CLS}(n, i)$ is quite simple to implement since:

- $y[j]$ is either $x[j]$ or $x[\text{mod}(j - i, n)]$.
- So all one needs is a MUX-gate to select between $x[j]$ or $x[\text{mod}(j - i, n)]$.
- The selection is based on the value of s .
- It follows that the delay of $\text{CLS}(n, i)$ is the delay of a MUX, and the cost is n times the cost of a MUX.


 


Figure: A row of multiplexers implement a $\text{CLS}(4, 2)$.

$CLS(n, i)$

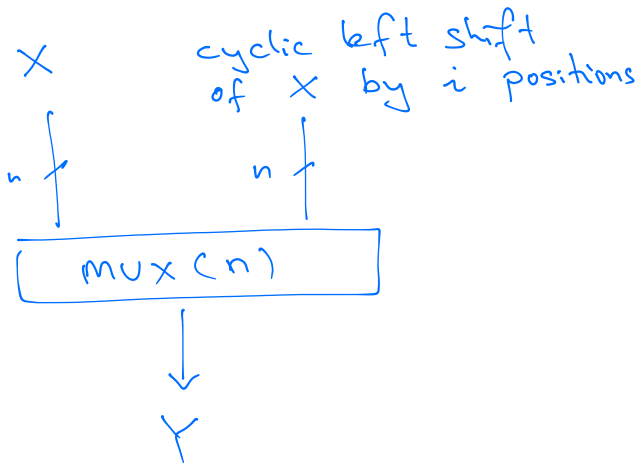

Back to BARREL-SHIFTER(n)

- The design of a BARREL-SHIFTER(n) is based on CLS($n, 2^i$) shifters.
- The implementation is based on k levels of CLS($n, 2^i$), for $i \in [k - 1 : 0]$.
- The i th level is controlled by $sa[i]$.

 


Figure: A BARREL-SHIFTER(n) built of k levels of CLS($n, 2^i$) ($n = 2^k$).

Observation

For every $x, q \in \mathbb{Z}$,

exercise

$$\text{mod}(x, n) = \text{mod}(x + qn, n).$$

Observation

If $\alpha = \text{mod}(a, n)$ and $\beta = \text{mod}(b, n)$, then

** CH 5 (bin. repr)
slide # 5*

$$\text{mod}(a - b, n) = \text{mod}(\alpha - \beta, n).$$


Claim

The barrel shifter design depicted in the previous slide is correct.

Proof.

Prove by induction on i , that output of $\text{CLS}(n, 2^i)$ equals the cyclic left shift of x by $\langle sa[i : 0] \rangle$. □

basis:

 

$i = 0$ $\gamma = \text{shift of } x \text{ by } \text{SA}[0] \text{ positions}$


hyp:

$\gamma = \text{shift of } x \text{ by } \langle \text{SA}[i:0] \rangle \text{ pos.}$

step:

$Z = \text{shift of } \gamma \text{ by } 2^{i+1} \cdot \text{SA}[i+1] \text{ pos.}$

 $= \text{shift of } x \text{ by } \langle \text{SA}[i:0] \rangle + 2^{i+1} \cdot \text{SA}[i+1] \text{ pos.} = \text{shift by } \langle \text{SA}[i+1:0] \rangle \text{ pos.} \quad \square$



Claim

The cost and delay of BARREL-SHIFTER(n) satisfy:

$$c(\text{BARREL-SHIFTER}(n)) = n \log_2 n \cdot c(\text{MUX})$$

$$d(\text{BARREL-SHIFTER}(n)) = \log_2 n \cdot d(\text{MUX}).$$

Proof.

Follows from the fact that the design consists of $\log_2 n$ levels of $\text{CLS}(n, 2^i)$ shifters. □

The cone of the Barrel Shifter

Consider the output $y[0]$ of $\text{BARREL-SHIFTER}(n)$.

Claim

The cone of the Boolean function implemented by the output $y[0]$ contains at least n elements.

Corollary

The delay of $\text{BARREL-SHIFTER}(n)$ is asymptotically optimal.


$$x[i] \in \text{cone}(y[0]) : \langle SA \rangle = n-i \Rightarrow y[0] = x[i]$$

Logical Shift

Definition

The binary string $y[n-1:0]$ is a **logical left shift** by ℓ positions of the binary string $x[n-1:0]$ if
 
$$y[i] \triangleq \begin{cases} 0 & \text{if } i < \ell \\ x[i - \ell] & \text{if } \ell \leq i < n. \end{cases}$$



Example

$y[3:0] = 0100$ is a logical left shift of $x[3:0] = 1001$ by $\ell = 2$ positions. When we apply a logical left shift to $x[n-1:0]$ by ℓ positions, we obtain the string $x[n-1-\ell:0] \circ 0^\ell$.

Fast multiplication

In binary representation, logical shifting to the left by s positions corresponds to multiplying by 2^s followed by modulo 2^n .

Logical Shifters (cont.)

Definition

The binary string $y[n-1:0]$ is a **logical right shift** by l positions of the binary string $x[n-1:0]$ if

$$y[i] \triangleq \begin{cases} 0 & \text{if } i \geq n-l \\ x[i+l] & \text{if } 0 \leq i < n-l. \end{cases}$$



Example

$y[3:0] = 0010$ is a logical right shift of $x[3:0] = 1001$ by $l = 2$ positions. When we apply a logical right shift to $x[n-1:0]$ by l positions, we obtain the string $0^l \circ x[n-1:l]$.

Fast division

In binary representation, logical shifting to the right by s positions corresponds to the integer part of the quotient after division by 2^s .

- Let $\text{LLS}(\vec{x}, i)$ denote the logical left shift of \vec{x} by i positions.
- Let $\text{LRS}(\vec{x}, i)$ denote the logical right shift of \vec{x} by i positions.

A bi-directional logical shifter

Definition

A $L\text{-SHIFT}(n)$ is a combinational circuit defined as follows:

Input:

- $x[n-1:0] \in \{0,1\}^n$,
- $sa[k-1:0] \in \{0,1\}^k$, where $k = \lceil \log_2 n \rceil$, and
- $\ell \in \{0,1\}$.

Output: $y[n-1:0] \in \{0,1\}^n$.

$\ell=1$ left shift
 $\ell=0$ right shift

Functionality: The output \vec{y} satisfies

$$\vec{y} \triangleq \begin{cases} \text{LLS}(\vec{x}, \langle \vec{sa} \rangle) & \text{if } \ell = 1, \\ \text{LRS}(\vec{x}, \langle \vec{sa} \rangle) & \text{if } \ell = 0. \end{cases}$$

Question

Design a bi-directional shifter using a left shifter and a right shifter (and select the answer based on ℓ).

A bi-directional logical shifter (cont.)

Example

- let $x[3 : 0] = 0010$.
- If $sa[1 : 0] = 10$ and $\ell = 1$, then $L\text{-SHIFT}(4)$ outputs $y[3 : 0] = 1000$.
- If $\ell = 0$, then the output equals $y[3 : 0] = 0000$.

Implementation

As in the case of cyclic shifters, we break the task of designing a logical shifter into sub-tasks of logical shifts by powers of two.

Definition

An $\text{LBS}(n, i)$ is a combinational circuit defined as follows:

Input: $x[n-1:0]$ and $s, \ell \in \{0, 1\}$.

Output: $y[n-1:0]$.

Functionality: The output \vec{y} satisfies

$$\vec{y} \triangleq \begin{cases} \vec{x} & \text{if } s = 0, \\ \text{LLS}(\vec{x}, i) & \text{if } s = 1 \text{ and } \ell = 1, \\ \text{LRS}(\vec{x}, i) & \text{if } s = 1 \text{ and } \ell = 0. \end{cases}$$

The role of the input s is to determine if a shift (in either direction) takes place at all. If $s = 0$, then $y[j] = x[j]$, and no shift takes place. If $s = 1$, then the direction of the shift is determined by ℓ .

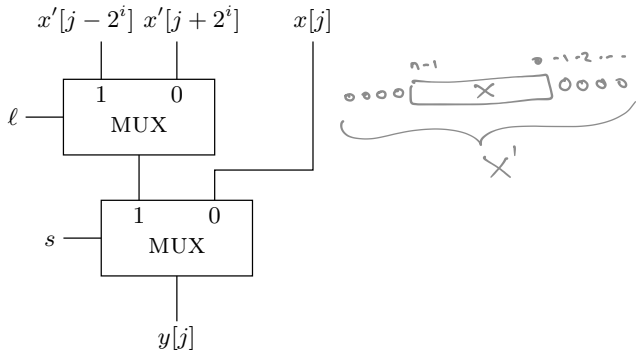


Figure: A bit-slice of an implementation of LBS($n, 2^i$).

question

Design a bi-directional logical shifter L-SHIFT(n) by cascading LBS($n, 2^i$) shifters.

Reduction of right shift to left shift

Definition

Let $rev : \{0, 1\}^* \rightarrow \{0, 1\}^*$ denote the function that reverses strings. Formally:

$$rev(A_{n-1}, \dots, A_1, A_0) = (A_0, A_1, \dots, A_n).$$

Reversing a string can be implemented with zero cost and zero delay. All one needs to do is connect input $A[i]$ to the output $B[n - i]$.

$$rev(011) = 110$$




zero cost
zero delay


Reduction of right shift to left shift (cont.)

Claim
 
$$\text{LRS}(\vec{x}, i) = \text{rev}(\text{LLS}(\text{rev}(\vec{x}), i)).$$



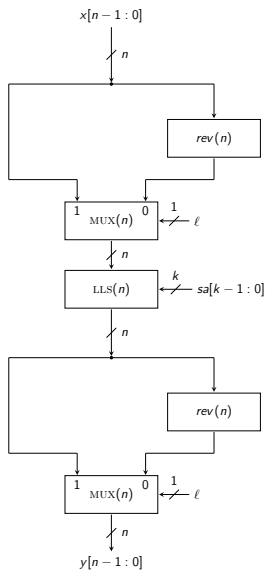bi-directional
logical
shifter
(left/right)




Arithmetic Shifters

Arithmetic shifters are used for shifting binary strings that represent signed integers in two's complement representation. **Since left shifting is the same in logical shifting and in arithmetic shifting, we discuss only right shifting** (i.e., division by a power of 2).

Definition

The binary string $y[n-1:0]$ is an **arithmetic right shift** by ℓ positions of the binary string $x[n-1:0]$ if the following holds:
 
$$y[i] \triangleq \begin{cases} x[n-1] & \text{if } i \geq n-\ell \\ x[i+\ell] & \text{if } 0 \leq i < n-\ell. \end{cases}$$



Example

- $y[3 : 0] = 0010$ is an arithmetic shift of $x[3 : 0] = 0101$ by $\ell = -1$ positions.
- On the other hand, $y[3 : 0] = 1110$ is an arithmetic shift of $x[3 : 0] = 1001$ by $\ell = -2$ positions.
- When we apply an arithmetic shift by $\ell < 0$ positions to $x[n - 1 : 0]$, we obtain the string $x[n - 1]^\ell \circ x[n - 1 : \ell]$.

Notation.

Let $\text{ARS}(\vec{x}, i)$ denote the arithmetic right shift of \vec{x} by i positions.

An arithmetic right shifter

Definition

An ARITH-SHIFT(n) is a combinational circuit defined as follows:

Input: $x[n-1:0] \in \{0,1\}^n$ and $sa[k-1:0] \in \{0,1\}^k$,
where $k = \lceil \log_2 n \rceil$.

Output: $y[n-1:0] \in \{0,1\}^n$.

Functionality: The output \vec{y} is a (sign-extended) arithmetic right shift of \vec{x} by $\langle \vec{sa} \rangle$ positions. Formally,

$$y[n-1:0] \triangleq \text{ARS}(x[n-1:0], \langle \vec{sa} \rangle).$$

Example

Let $x[3:0] = 1001$. If $sa[1:0] = 10$, then ARITH-SHIFT(4) outputs $y[3:0] = 1110$.

question

Design an arithmetic right shifter ARITH-SHIFT(n).