

Digital Logic Design: a rigorous approach ©

Chapter 15: Addition

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

May 21, 2020

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

Definition of a binary adder

Definition

ADDER(n) - a **binary adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$.

Functionality:

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]. \quad (1)$$

Addition terminology:

- addends: $\langle \vec{A} \rangle = \sum_{i=1}^{n-1} A[i] \cdot 2^i$, and $\langle \vec{B} \rangle = \sum_{i=1}^{n-1} B[i] \cdot 2^i$
- carry-in bit : $C[0]$
- sum: $\langle \vec{S} \rangle$
- carry-out bit: $C[n]$

binary adder definition (cont)

Definition

$\text{ADDER}(n)$ - a **binary adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$.

Functionality:

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]. \quad (2)$$

Claim ($\text{ADDER}(n)$ is well defined)

For every $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$, there exist $S[n-1:0] \in \{0,1\}^n$ and $C[n] \in \{0,1\}$ such that

$$\langle \vec{S} \rangle + 2^n \cdot C[n] = \langle \vec{A} \rangle + \langle \vec{B} \rangle + C[0]$$

Full Adder

An ADDER(1) is called a **full adder**.

Definition (Full-Adder)

FA - a **Full-Adder** is a combinational circuit with 3 inputs $x, y, z \in \{0, 1\}$ and 2 outputs $c, s \in \{0, 1\}$ that satisfies:

$$2c + s = x + y + z.$$


Terminology: s -**sum output**, c -**carry-out output**.

Claim

$$s = x \oplus y \oplus z,$$

$$c = (x \cdot y) \vee (y \cdot z) \vee (x \cdot z).$$

Ripple Carry Adder $RCA(n)$

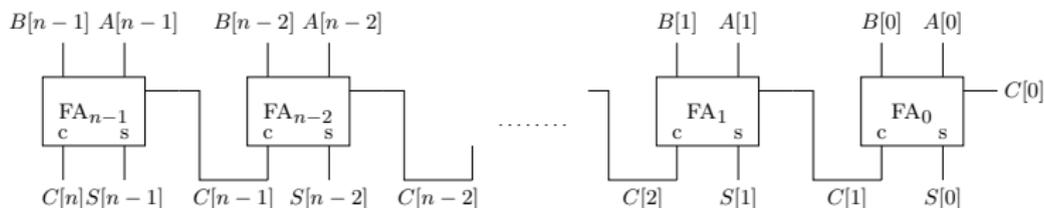


- same addition algorithm that we use for adding numbers by hand.
- row of n Full-Adders connected in a chain.
- the weight of every signal is two to the power of its index. (Do not confuse weight here with Hamming weight. Weight means here the value in binary representation.)

Recursive definition of $RCA(n)$


Basis: an $RCA(1)$ is simply a Full-Adder.

Reduction Step:

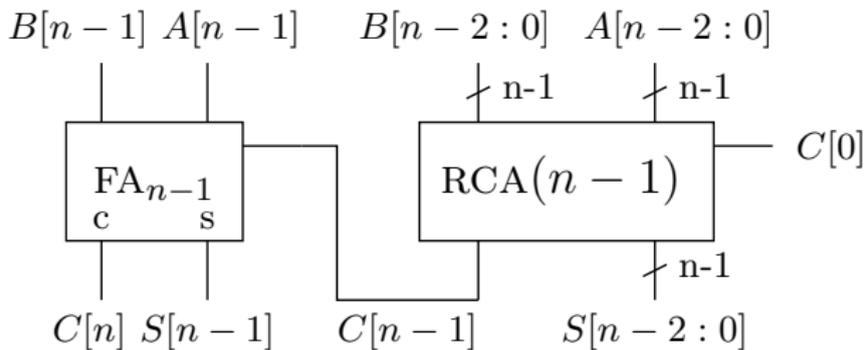

Claim

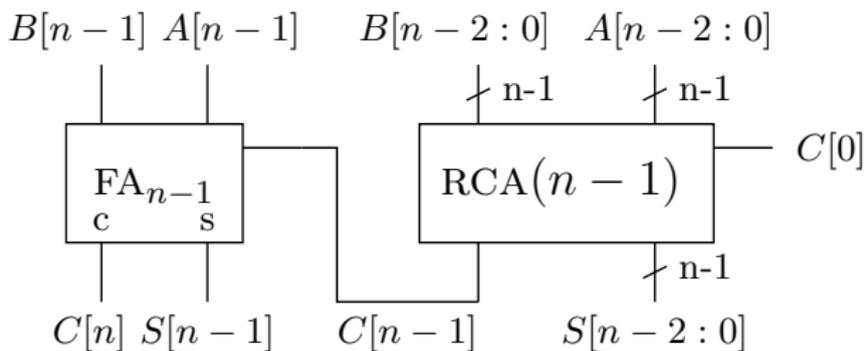RCA(n) is a correct implementation of ADDER(n).



Delay and cost analysis

The cost of an $RCA(n)$ satisfies:

$$c(RCA(n)) = n \cdot c(FA) = \Theta(n).$$

The delay of an $RCA(n)$ satisfies

$$d(RCA(n)) = n \cdot d(FA) = \Theta(n).$$

Clock rates in modern microprocessors correspond to the delay of 15-20 gates (in more aggressive designs, the critical paths are even shorter). Most microprocessors easily add 32-bit numbers within one clock cycle (high-end microprocessors even add 100-bit number in a cycle). Obviously, adders in such microprocessors are not Ripple Carry Adders.


Carry bits

We now define the carry bits associated with the addition

$$\langle A[n-1:0] \rangle + \langle B[n-1:0] \rangle + C[0] = \langle S[n-1:0] \rangle + 2^n \cdot C[n]$$

Definition

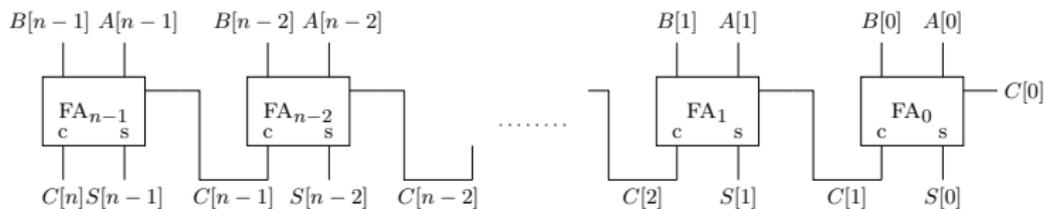The carry bits $C[n:0]$ are defined as the values of the stable signals $C[n:0]$ in an $\text{RCA}(n)$.



This definition is well defined in light of the Simulation Theorem of combinational circuits.

Cone of adder outputs

The correctness proof of $\text{RCA}(n)$ implies that, for every $0 \leq i \leq n - 1$,

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0] = 2^{i+1} \cdot C[i + 1] + \langle S[i : 0] \rangle.$$

Hence, for every $0 \leq i \leq n - 1$:

$$\begin{aligned} C[i + 1] = 1 &\iff \langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0] \geq 2^{i+1} \\ &\quad \langle S[i : 0] \rangle = \text{mod}(\langle A[i : 0] \rangle + \langle B[i : 0] \rangle + C[0], 2^{i+1}). \end{aligned}$$

Claim

For each $0 \leq i \leq n - 1$, the cone of Boolean functions corresponding to $C[i + 1]$ and $S[i]$ consists of $2i + 3$ inputs corresponding to $A[i : 0]$, $B[i : 0]$, and $C[0]$.

Claim



Let A denote a combinational circuit that implements an $\text{ADDER}(n)$. If the fan-in in C is at most 2, then

$$c(A) \geq 2n,$$

$$d(A) \geq \log_2(2n + 1).$$

Compare with the cost and delay of $\text{RCA}(n)$.


Conditional Sum Adder - motivation

 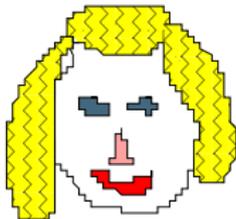


Conditional Sum Adder - motivation




Conditional Sum Adder - motivation

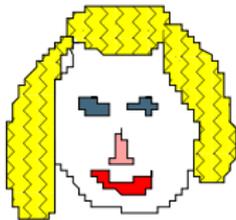


Alice,
Let's have some fun!

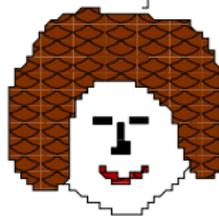

Conditional Sum Adder - motivation

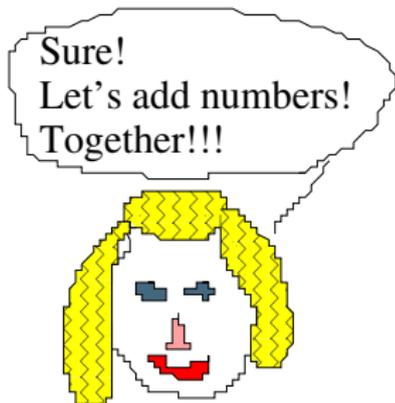


Conditional Sum Adder - motivation

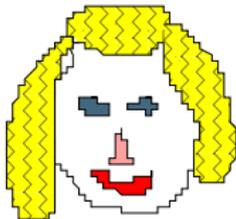

Never done that before!
Let's try...




Conditional Sum Adder - motivation

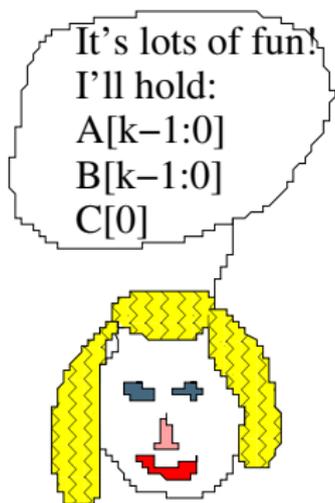

Conditional Sum Adder - motivation

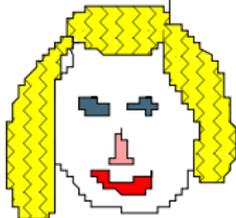It's lots of fun!
I'll hold:
 $A[k-1:0]$
 $B[k-1:0]$
 $C[0]$




and I'll hold:
 $A[n-1:k]$
 $B[n-1:k]$




Conditional Sum Adder - motivation

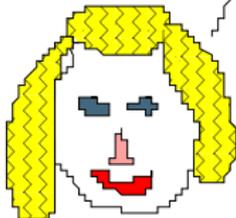The rules are:
-at the end we must
know the sum.
-it doesn't matter who
has which sum bits.



Conditional Sum Adder - motivation


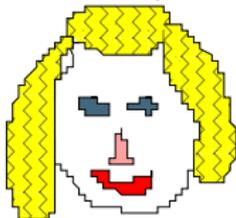
-communication is costly,
and
-our goal is to compute the
sum asap.




Conditional Sum Adder - motivation




Conditional Sum Adder - motivation

 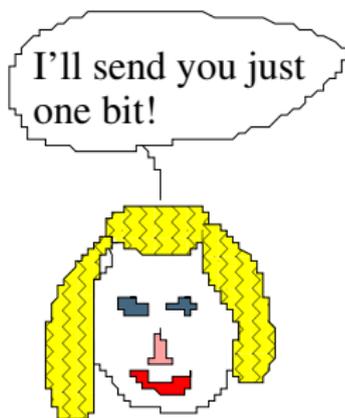

Conditional Sum Adder - motivation

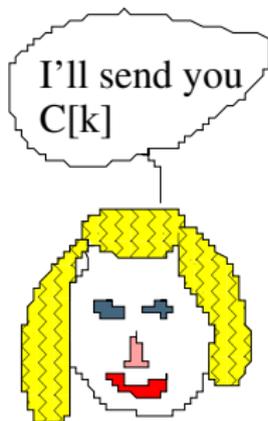


Conditional Sum Adder - motivation

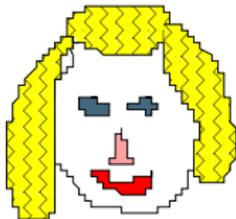

*It's taking her a while...
Is there anything I could
do in the meantime?*




Conditional Sum Adder - motivation

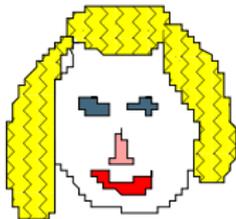

*I have an idea:
Her message will be
either zero or one...*




Conditional Sum Adder - motivation

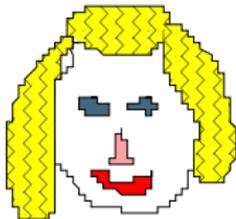

*So I will compute my
answers for both cases...*




Conditional Sum Adder - motivation

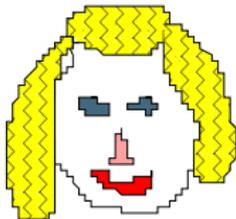


*As soon as $C[k]$ arrives,
I'll select one of my
pre-computed answers!*




Conditional Sum Adder - motivation

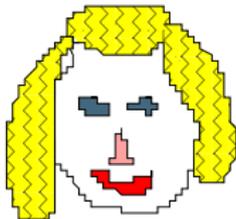

 Alice,
I have to tell you,
This game is FUN!!!



Conditional Sum Adder - motivation

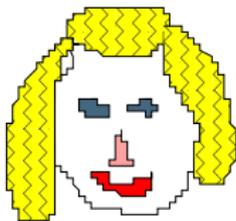


It reminds me of this
course I took once...



Conditional Sum Adder $CSA(n)$

basis: A $CSA(1)$ is simply a Full-Adder.

reduction step:

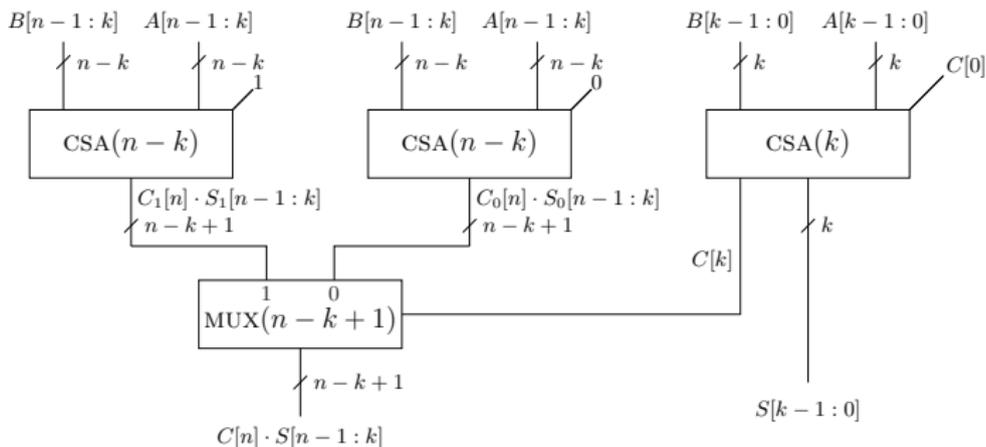

Claim

The $CSA(n)$ is a correct $ADDER(n)$ design.

Delay analysis

To simplify the analysis we assume that $n = 2^\ell$. To optimize the delay, we use $k = n/2$.

Let $d(\text{FA})$ denote the delay of a Full-Adder. The delay of a $\text{CSA}(n)$ satisfies the following recurrence:

$$d(\text{CSA}(n)) = \begin{cases} d(\text{FA}) & \text{if } n = 1 \\ d(\text{CSA}(n/2)) + d(\text{MUX}) & \text{otherwise.} \end{cases}$$

Hence, the delay of a $\text{CSA}(n)$ is

$$\begin{aligned} d(\text{CSA}(n)) &= \ell \cdot d(\text{MUX}) + d(\text{FA}) \\ &= \Theta(\log n). \end{aligned}$$

Let $c(\text{FA})$ denote the cost of a Full-Adder. The cost of a $\text{CSA}(n)$ satisfies the following recurrence:

$$c(\text{CSA}(n)) = \begin{cases} c(\text{FA}) & \text{if } n = 1 \\ 3 \cdot c(\text{CSA}(n/2)) + (n/2 + 1) \cdot c(\text{MUX}) & \text{otherwise.} \end{cases}$$

the solution of this recurrence is $c(\text{CSA}(n)) = \Theta(n^{\log_2 3})$.

- $\log_2 3 \approx 1.58$, so a $\text{CSA}(n)$ is costly.
- but delay is logarithmic!
- the $\text{CSA}(n)$ design uses three half-size adders (easy to use).

Definition

COMP-ADDER(n) - a **Compound Adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0, 1\}^n$.

Output: $S[n:0], T[n:0] \in \{0, 1\}^{n+1}$.

Functionality:

$$\langle \vec{S} \rangle = \langle \vec{A} \rangle + \langle \vec{B} \rangle$$


$$\langle \vec{T} \rangle = \langle \vec{A} \rangle + \langle \vec{B} \rangle + 1.$$

Note that a Compound Adder does not have carry-in input. To simplify notation, the carry-out bits are denoted by $S[n]$ for the sum and by $T[n]$ for the incremented sum.


COMP-ADDER(n) - Implementation

basis: $n = 1$, we simply use a Full-Adder and a Half-Adder.

reduction step:

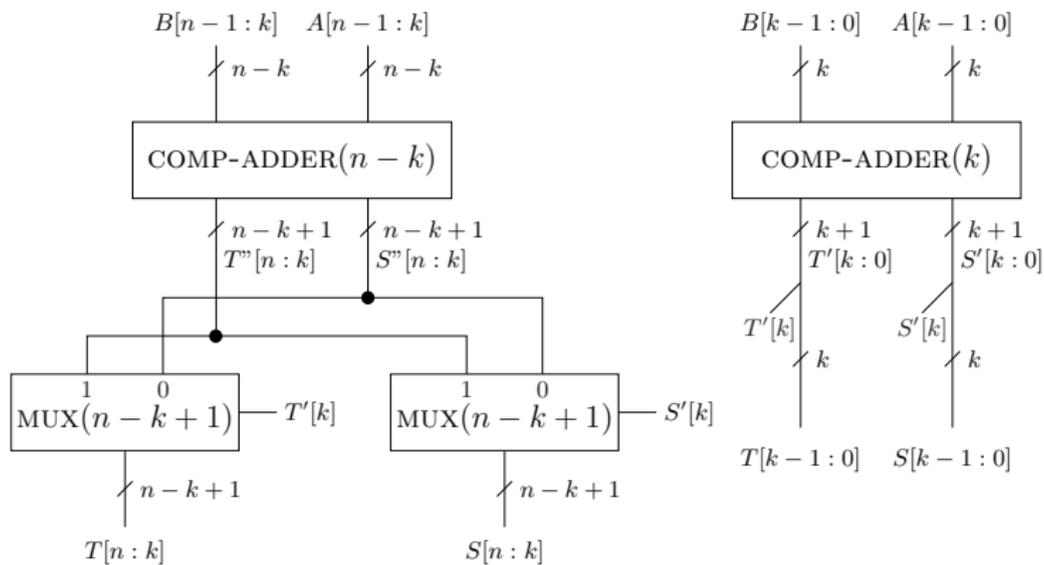


COMP-ADDER(n) - example

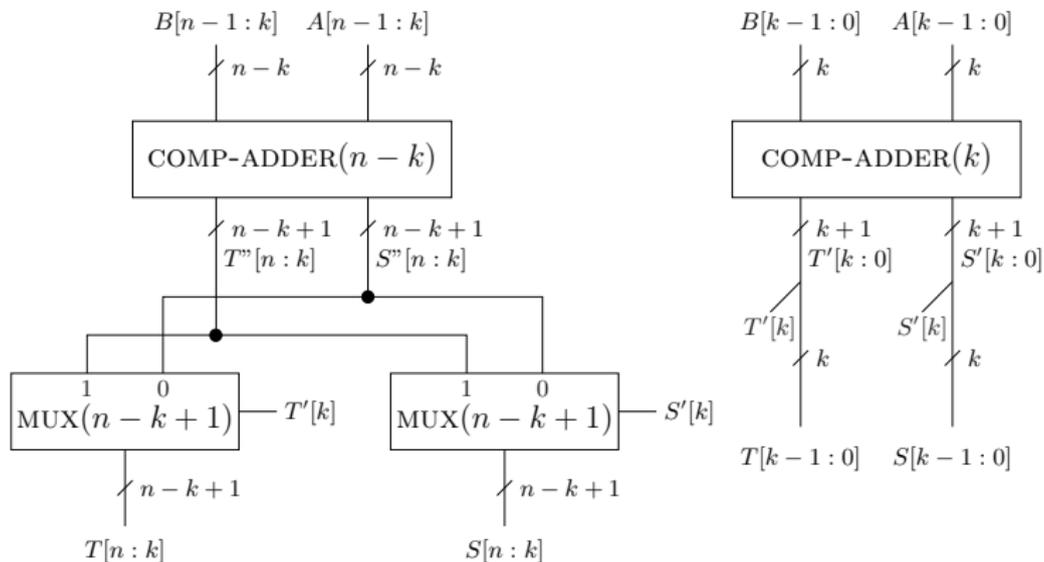

Example

Consider a COMP-ADDER(4) with input $A[3:0] = 0110$ and $B[3:0] = 1001$.

COMP-ADDER(n) - example

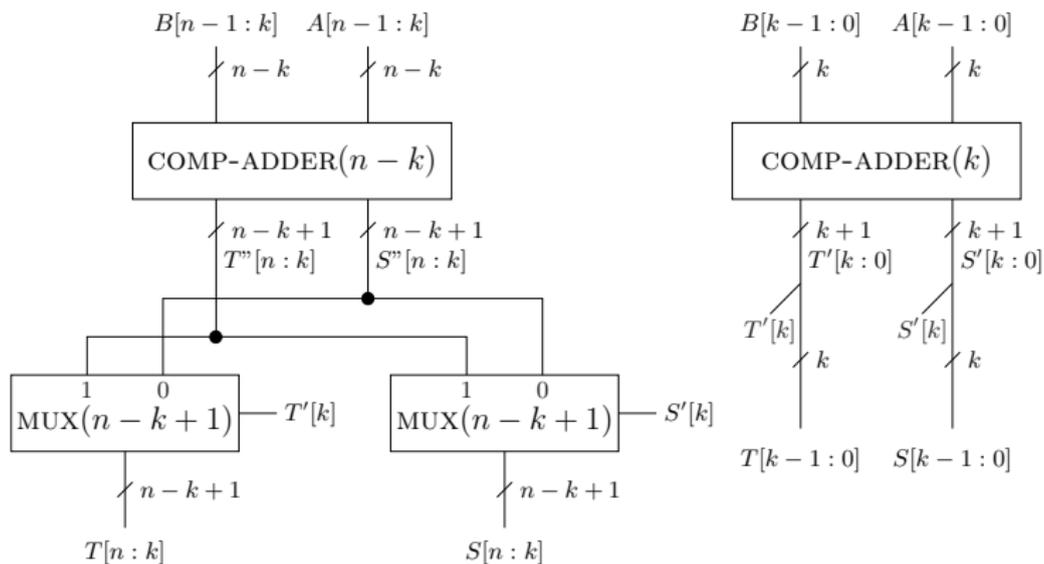

Claim

The COMP-ADDER(n) design is a correct adder.

Delay analysis

To simplify the analysis we assume that $n = 2^\ell$. To optimize the delay, we use $k = n/2$.

The delay of a $\text{COMP-ADDER}(n)$ satisfies the following recurrence:

$$d(\text{COMP-ADDER}(n)) = \begin{cases} d(\text{FA}) & \text{if } n = 1 \\ d(\text{COMP-ADDER}(n/2)) + d(\text{MUX}) & \text{otherwise.} \end{cases}$$

Hence,

$$\begin{aligned} d(\text{COMP-ADDER}(n)) &= \ell \cdot d(\text{MUX}) + d(\text{FA}) \\ &= \Theta(\log n). \end{aligned}$$

The cost of a $\text{COMP-ADDER}(n)$ satisfies the following recurrence:

$$c(\text{COMP-ADDER}(n)) = \begin{cases} c(\text{FA}) + c(\text{HA}) \\ 2 \cdot c(\text{COMP-ADDER}(n/2)) + (n/2 + 1) \cdot c(\text{MUX}) \end{cases}$$

Hence, $c(\text{COMP-ADDER}) = \Theta(n \log n)$.

SURPRISE!!! $c(\text{COMP-ADDER}(n)) \ll c(\text{CSA}(n))$.

The correctness of $\text{RCA}(n)$ implies that, for every $0 \leq i \leq n - 1$,

$$S[i] = A[i] \oplus B[i] \oplus C[i] \quad (3)$$

By xoring $C[i] \oplus S[i]$ to both sides, we obtain,

$$C[i] = A[i] \oplus B[i] \oplus S[i] . \quad (4)$$

- defined binary addition.
- Three adder designs: Ripple Carry Adder, Conditional Sum Adder, Compound Adder.
- The problems of computing the sum bits and the carry bits are equivalent with respect to a constant-time linear-cost reduction. Since the cost of every adder is $\Omega(n)$ and the delay is $\Omega(\log n)$, we regard the problems of computing the sum bits and the carry bits as equivalently hard.
- Design methodology: divide & conquer.
- Surprise! $\text{COMP-ADDER}(n)$ is much cheaper asymptotically than a $\text{CSA}(n)$.
- Left to show: an adder with linear cost and logarithmic delay....