

Digital Logic Design: a rigorous approach ©  
Chapters 17-20: Flip-Flops, Synchronous Circuits, and Finite  
State Machines

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

December 21, 2021

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

# Preliminary questions


- ① How is time measured in a synchronous circuit?
- ② What is a “clock” in a microprocessor?
- ③ What is the frequency of a clock?
- ④ What is memory? How are bits stored?

# The clock

the clock is generated by rectifying and amplifying a signal generated by special non-digital devices (e.g., crystal oscillators).
 
## Definition

A **clock** is a periodic logical signal that oscillates instantaneously between logical one and logical zero. There are two instantaneous transitions in every clock period: (i) in the beginning of the clock period, the clock transitions instantaneously from zero to one; and (ii) at some time in the interior of the clock period, the clock transitions instantaneously from one to zero.



- A clock partitions time into discrete intervals.
- $t_i$  - the starting time of the  $i$ th clock cycle.
- $[t_i, t_{i+1})$  -clock cycle  $i$ .
- Clock period =  $t_{i+1} - t_i$ .

## Assumption

We assume that the clock period equals 1.

$$t_{i+1} = t_i + 1 .$$

## Definition

A **flip-flop** is defined as follows.

**Inputs:** Digital signals  $D(t)$  and a clock CLK.

**Output:** A digital signal  $Q(t)$ .

**Functionality:**

$$Q(t + 1) = D(t) .$$

$t$	$D[t]$	$Q[t]$
0	1	?
1	0	1
2	0	0
3	1	0
4	1	1

## Definition

A clock enabled flip-flop is defined as follows.

**Inputs:** Digital signals  $D(t)$ ,  $CE(t)$  and a clock  $CLK$ .



**Output:** A digital signal  $Q(t)$ .

**Functionality:**

$$Q(t + 1) = \begin{cases} D(t) & \text{if } CE(t) = 1 \\ Q(t) & \text{if } CE(t) = 0. \end{cases}$$

We refer to the input signal  $CE(t)$  as the clock-enable signal. Note that the input  $CE(t)$  indicates whether the flip-flop samples the input  $D(t)$  or maintains its previous value.
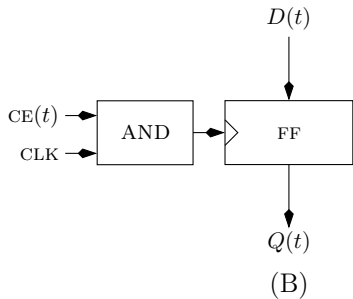 
# Which design is a correct clock enabled FF?



# The Zero Delay Model


- ① Transitions of all signals are instantaneous.
- ② Combinational gates:  $t_{pd} = t_{cont} = 0$ .
- ③ Flip-flops satisfy:

$$Q(t + 1) = D(t) .$$

- ④ Simplified model for specifying and simulating the functionality of circuits with flip-flops.
- ⑤ For a signal  $X$ , let  $X_i$  denote its value during the  $i$ th clock cycle.



# Example: Sequential XOR

 

$i$	$A_i$	$Y_i$	$Z_i$
0	0	0	0
1	0	0	0
2	1	1	0
3	0	1	1
4	0	1	1
5	1	0	1
6	0	0	0
7	1	1	0
8	0	1	1

## Definition

A *sequential adder* is defined as follows.

**Inputs:**  $A, B$  and a clock signal  $\text{CLK}$ , where  $A_i, B_i \in \{0, 1\}$ .

**Output:**  $S$ , where  $S_i \in \{0, 1\}$ .

**Functionality:** Then, for every  $i \geq 0$ ,

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle = \langle S[i : 0] \rangle \pmod{2^{i+1}}.$$

# Sequential Adder Implementation

# Sequential Adder: Correctness

## Theorem

$$\sum_{j=0}^i A_j \cdot 2^j + \sum_{j=0}^i B_j \cdot 2^j = \sum_{j=0}^i S_j \cdot 2^j + c_{out}(i) \cdot 2^{i+1}.$$

## Proof.

The proof is by induction on  $i$ .

The induction basis for  $i = 0$  follows from the functionality of the full-adder:

$$A_0 + B_0 + C_{in}(0) = 2 \cdot C_{out}(0) + S_0.$$

This requires that  $C_{in}(0) = 0$ ! Namely, that the FF is initialized to zero. (We will discuss how to partly mitigate the issue of initialization later.) □

# Sequential Adder: Implementation - correctness (cont.)


## Proof.

We now prove the induction step for  $i > 0$ .

$$\begin{aligned}\sum_{j=0}^i A_j \cdot 2^j + \sum_{j=0}^i B_j \cdot 2^j &= (A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} A_j \cdot 2^j + \sum_{j=0}^{i-1} B_j \cdot 2^j \\ &= (A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j + C_{out}(i-1) \cdot 2^i \\ &= (C_{in}(i) + A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j \\ &= (S_i + 2 \cdot C_{out}(i)) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j \\ &= \sum_{j=0}^i S_j \cdot 2^j + C_{out}(i) \cdot 2^{i+1}.\end{aligned}$$
 
# Relation between $RCA(n)$ and Sequential Adder

- 1  $FA_i$  is “simulated” by the FA (in Seq. Adder) in the  $i$ 'th clock cycle.
- 2 We can view  $RCA(n)$  as an “unrolling” of the Seq. Adder.



# Comparison with Combinational Lower Bounds

- ➊ Addition and  $\text{XOR}_n$  have functional cone of size  $n$ .
- ➋ Every combinational circuit has cost  $\Omega(n)$  and delay  $\Omega(\log n)$ .
- ➌ But sequential versions have cost  $O(1)$ ! How can that be?

A term **register** is used to define a memory device that stores a bit or more. There are two main types of register depending on how their contents are loaded.

- ① Parallel Load Register
- ② Shift Register (also called a serial load register)



## Definition

An  $n$ -bit *parallel load register* is specified as follows.

- Inputs:**
- $D[n - 1 : 0](t)$ ,
  - $CE(t)$ , and
  - a clock CLK.

**Output:**  $Q[n - 1 : 0](t)$ .

**Functionality:**

$$Q[n - 1 : 0](t + 1) = \begin{cases} D[n - 1 : 0](t) & \text{if } CE(t) = 1 \\ Q[n - 1 : 0](t) & \text{if } CE(t) = 0. \end{cases}$$

An  $n$ -bit parallel load register is simply built from  $n$  clock enabled flip-flops.

# Parallel Load Register - design


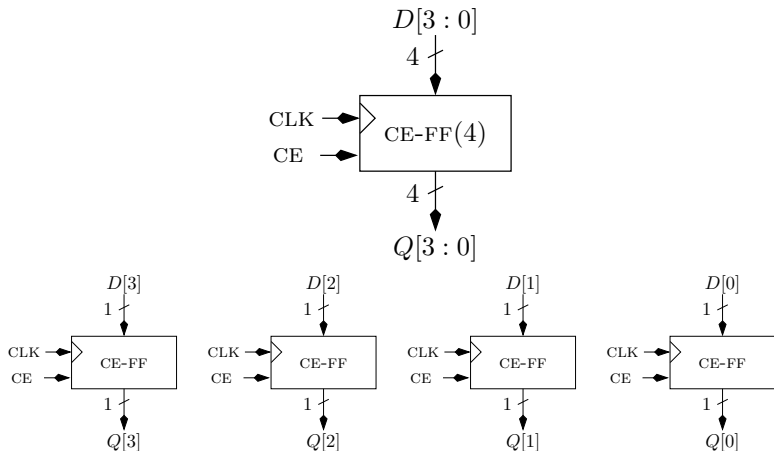


Figure: A 4-bit parallel load register

# Parallel Load Register - simulation

 

$i$	$D[3 : 0]$	CE	$Q[3 : 0]$
0	1010	1	0000
1	0101	1	1010
2	1100	0	0101
3	1100	1	0101
4	0011	1	1100

## Definition


A *shift register* of  $n$  bits is defined as follows.

**Inputs:**  $D[0](t)$  and a clock CLK.

**Output:**  $Q[n - 1](t)$ .


**Functionality:**  $Q[n - 1](t + n) = D[0](t)$ .

# Shift Register - design

 

**Figure:** A 4-bit shift register. Functionality:  $Q[3](t + 4) = D[0](t)$

# Shift Registers - simulation

 

$i$	$D[0]$	$Q[3 : 0]$
0	1	0000
1	1	0001
2	1	0011
3	0	0111
4	1	1110

## Definition


A ROM( $2^n$ ) that implements a Boolean function  $M : [0..2^n - 1] \rightarrow \{0, 1\}$  is defined as follows.

**Inputs:**  $Address[n - 1 : 0](t)$ .

**Output:**  $D_{out}(t)$ .

 **Functionality :**

$$D_{out} = M[\langle Address \rangle] .$$



# Read-Only Memory (ROM)

- The contents stored in each memory cell are preset and fixed.
- ROMs are used to store information that should not be changed.
- For example, the ROM stores the program that is executed when the computer is turned on.
- Modern computers use non-volatile memory as ROM (such memory does allow write operations - and writing is often limited by “permissions”)



# Random Access Memory (RAM)

- ① Hardware module that implements an array of memory cells, where each memory cell stores a single bit.
- ② In each cycle, a single memory cell is accessed.
- ③ Two operations are supported: read and write.
  - read operation: the contents of the accessed memory is output.
  - write operation: a new value is stored in the accessed memory cell.
- ④ The number of memory cells is denoted by  $2^n$ .
- ⑤ Each cell has a distinct address between 0 and  $2^n - 1$ .
- ⑥ The cell to be accessed is specified by an  $n$ -bit string called *Address*.
- ⑦ The array of memory cells is denoted by  $M[2^n - 1 : 0]$ . Let  $M[i](t)$  denote the value stored in the  $i$ th entry of the array  $M$  during clock cycle  $t$ .

## Definition

A RAM( $2^n$ ) is specified as follows.

**Inputs:**  $Address[n - 1 : 0](t) \in \{0, 1\}^n, D_{in}(t) \in \{0, 1\},$   
 $R/\overline{W}(t) \in \{0, 1\}$  and a clock CLK.

**Output:**  $D_{out}(t) \in \{0, 1\}.$

**Functionality :**

- ① data: array  $M[2^n - 1 : 0]$  of bits.
- ② initialize:  $\forall i : M[i] \leftarrow 0.$
- ③ For  $t = 0$  to  $\infty$  do
  - ①  $D_{out}(t) = M[\langle Address \rangle](t).$
  - ② For all  $i \neq \langle Address \rangle : M[i](t + 1) \leftarrow M[i](t).$
  - ③

$$M[\langle Address \rangle](t + 1) \leftarrow \begin{cases} D_{in}(t) & \text{if } R/\overline{W}(t) = 0 \\ M[\langle Address \rangle](t) & \text{else.} \end{cases}$$


 


Figure: A schematic of a  $\text{RAM}(2^n)$ .

# RAM -design

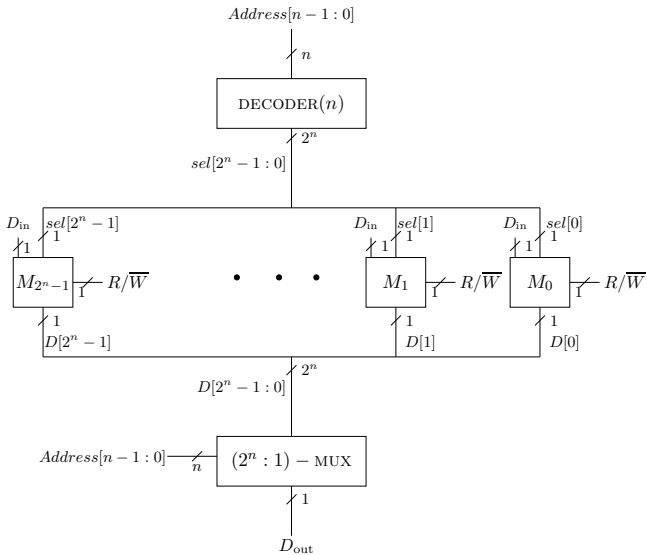

## Definition

A single bit *memory cell* is defined as follows.

**Inputs:**  $D_{\text{in}}(t)$ ,  $R/\overline{W}(t)$ ,  $\text{sel}(t)$ , and a clock CLK.

**Output:**  $D_{\text{out}}(t)$ .

**Functionality:**

Assume that  $D_{\text{out}}$  is initialized zero, i.e.,  $D_{\text{out}}(0) = 0$ . The functionality is defined according to the following cases.

$$D_{\text{out}}(t + 1) \leftarrow \begin{cases} D_{\text{in}}(t) & \text{if } \text{sel}(t) = 1 \text{ and } R/\overline{W}(t) = 0 \\ D_{\text{out}}(t) & \text{otherwise.} \end{cases}$$

# Memory Cell - design

 


Figure: An implementation of a memory cell.

# Summary of Part 1

- Clock signal & clock cycles.
- Flip-Flops and clock-enabled FF's
- Examples:
  - ① Sequential XOR
  - ② Sequential Adder
  - ③ Comparison with combinational lower bounds.
- Registers: parallel load and shift registers.
- ROM and RAM.

# Preliminary questions

- 1 What is a synchronous circuit?
- 2 How can we initialize a synchronous circuit?



# Synchronous Circuits

- Building blocks: combinational gates, wires, and flip-flops.
- The graph  $G$  of a synchronous circuit is directed but may contain cycles (e.g., sequential adder).
- A flip-flop has two inputs  $D$  and  $CLK$  that play quite different roles. We must make sure that we know the input port of each incoming edge.
- Definition based on a reduction to a combinational circuit...

## Definition


A **synchronous circuit** is a circuit  $C$  composed of combinational gates, wires, and flip-flops that satisfies the following conditions:

- 1 There is an input gate that feeds the clock signal  $CLK$ .
- 2 The set of ports that are fed by the clock  $CLK$  equals the set of clock-inputs of the flip-flops.
- 3 Let  $C'$  denote a circuit obtained from  $C$  by **stripping the flip-flops away**. Then, the circuit  $C'$  is a combinational circuit.

## Definition

- 1 Delete the input gate that feeds the clock `CLK` and all the wires carrying the clock signal.
- 2 Remove all the flip-flops.
- 3 Add an output gate for each  $D$  port.
- 4 Add an input gate for each  $Q$  port.

## Example - stripping FFs away

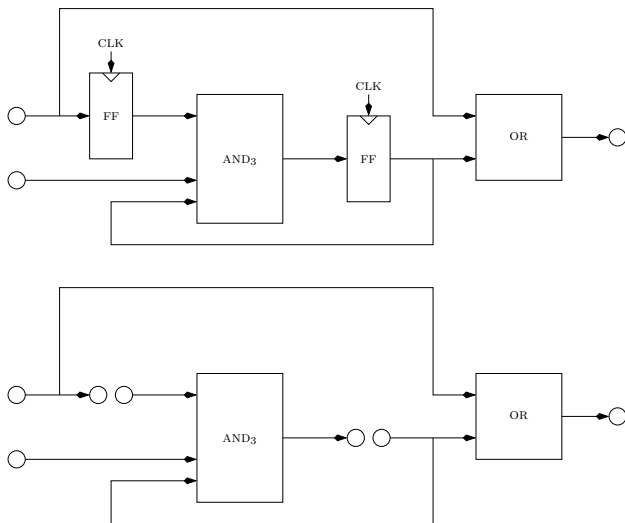

**Figure:** A synchronous circuit  $C$  and the combinational circuit  $C'$  obtained from  $C$  by stripping away the flip-flops.

It is easy to check if a given circuit  $C$  is a synchronous circuit.

- Check if there is a clock signal that is connected to all the clock terminals of the flip-flops and only to them.
- Strip the flip-flops away to obtain the circuit  $C'$ . Check if  $C'$  is a combinational circuit.

# Cycles (closed paths) in a synchronous circuit

## Claim

*Every closed path in a synchronous circuit traverses at least one flip-flop.*

Assumptions:

- Initialization (magical?): For every flip-flop  $FF_i$ , let  $S_0(FF_i) \in \{0, 1\}$  denote the value output by  $FF_i$  in clock cycle  $t = 0$ .
- Input sequence: For every input gate  $X$  let  $IN_t(X) \in \{0, 1\}$  the input fed by  $X$  in clock cycle  $t$ .

Initialization serves a crucial role in the induction basis!

---

**Algorithm 1**  $\text{SIM}(C, S_0, \{IN_t\}_{t=0}^{T-1})$  - An algorithm for simulating a synchronous circuit  $C$  with respect to an initialization  $S_0$  and a sequence of inputs  $\{IN_t\}_{t=0}^{T-1}$ .

---

- ① Construct the combinational circuit  $C'$  obtained from  $C$  by stripping away the flip-flops.
  - ② For  $t = 0$  to  $T - 1$  do:
    - ① Simulate the combinational circuit  $C'$  with input values corresponding to  $S_t$  and  $IN_t$ . Namely, every input gate in  $C$  feeds a value according to  $IN_t$ , and every  $Q$ -port of a flip-flop feeds a value according to  $S_t$ . For every sink  $z$  in  $C'$ , let  $z_t$  denote the value fed to  $z$  according to this simulation.
    - ② For every  $Q$ -port  $S$  of a flip-flop, define  $S_{t+1} \leftarrow NS_t$ , where  $NS$  denotes the  $D$ -port of the flip-flop.
-



# The Canonic Form of a Synchronous Circuit

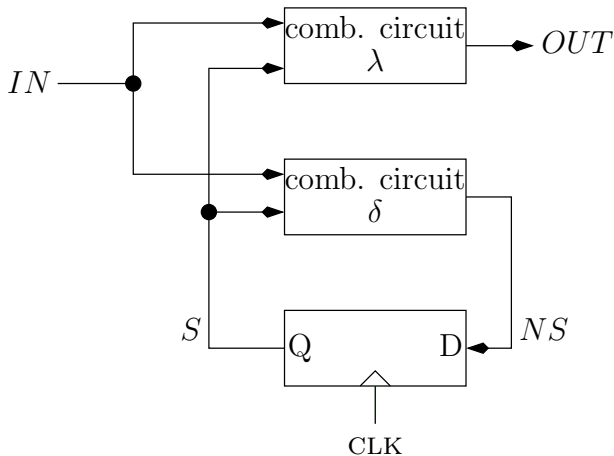


Figure: A synchronous circuit in canonic form.


# Initialization

- We require that the output of every flip-flop be defined during the first clock cycle. Impossible?
  - ① How can we even define the “first” clock cycle?
  - ② What is the state of a flip-flop after power on?
  - ③ How can anything be set or determined after power on?
- Deus ex machina: introduce a **reset signal**:

$$\text{reset}(t) \triangleq \begin{cases} 1 & \text{if } t = 0, \\ 0 & \text{otherwise.} \end{cases}$$

- How is a reset signal generated? How could a reset signal differ from the the output of a flip-flop?
- **No solution to this problem within the digital abstraction.** All we can try to do is reduce the probability of such an event.
- In practice, a special circuit, called a **reset controller**, generates a proper reset signal with very high probability. Oddly enough, a reset controller is usually constructed by cascading flip-flops!

# Using the reset

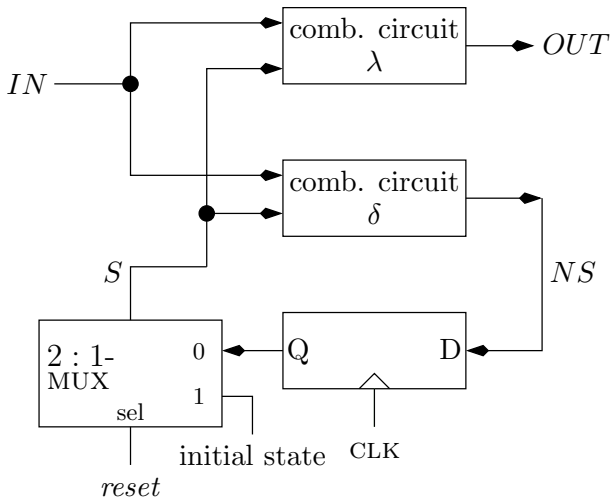

Restart “time”: If  $reset(t) = 1$ , then set  $t \leftarrow 0$ .

# Functionality: the canonic form

We denote the logical value of a signal  $X$  during the  $i$ 'th clock cycle by  $X_i$ .

## Claim


For every  $i \geq 0$ :

$$S_i = \begin{cases} \text{initial state} & \text{if } i = 0 \\ NS_{i-1} & \text{if } i \geq 1 \end{cases}$$

$$NS_i = \delta(IN_i, S_i)$$

$$OUT_i = \lambda(IN_i, S_i)$$

# Sequential Adder with Reset

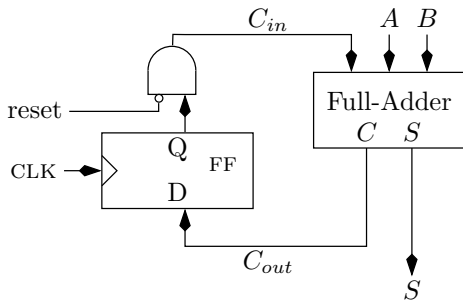

Note: Mux controlled by reset implemented by an AND-gate.

# Sequential Adder with Reset

What happens if  $|\{t \mid \text{reset}(t) = 1\}| > 1$ ? If  $\text{reset}(t) = 1$ , then we forget about the past, we treat clock cycle  $t$  as the first clock cycle. Formally, we define the last initialization  $r(i)$  as follows:

$$r(i) \triangleq \max\{t \leq i : \text{reset}(t) = 1\}.$$

Namely,  $r(i)$  specifies the **last** time  $\text{reset}(t) = 1$  not after cycle  $i$ . If  $\text{reset}_j = 0$ , for every  $j \leq i$ , then  $r(i)$  is not defined, and functionality is unspecified. If  $r(i)$  is well defined, then the functionality is that, for every  $i \geq 0$ ,

$$\langle A[i : r(i)] \rangle + \langle B[i : r(i)] \rangle = \langle S[i : r(i)] \rangle \pmod{2^{i-r(i)+1}}.$$

The functionality of a synchronous circuit in the canonic form is so important that it justifies a term called **finite state machines**.

## Definition

A **finite state machine** (FSM) is a 6-tuple  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ , where

- $Q$  is a set of **states**.
- $\Sigma$  is the alphabet of the input.
- $\Delta$  is the alphabet of the output.
- $\delta : Q \times \Sigma \rightarrow Q$  is a **transition function**.
- $\lambda : Q \times \Sigma \rightarrow \Delta$  is an **output function**.
- $q_0 \in Q$  is an **initial state**.

# What does an FSM do?

An FSM is an abstract machine that operates as follows. The input is a sequence  $\{x_i\}_{i=0}^{n-1}$  of symbols over the alphabet  $\Sigma$ . The output is a sequence  $\{y_i\}_{i=0}^{n-1}$  of symbols over the alphabet  $\Delta$ . An FSM transitions through the sequence of states  $\{q_i\}_{i=0}^n$ . The state  $q_i$  is defined recursively as follows:

$$q_{i+1} \triangleq \delta(q_i, x_i)$$

The output  $y_i$  is defined as follows:

$$y_i \triangleq \lambda(q_i, x_i).$$



Other terms for a finite state machine are a **finite automaton with outputs** and **transducer**. In the literature, an FSM according to our definition is often called a **Mealy Machine**. Another type of machine, called **Moore Machine**, is an FSM in which the domain of output function  $\lambda$  is  $Q$  (namely, the output is only a function of the state and does not depend on the input).

# State Diagrams

FSMs are often depicted using state diagrams.

## Definition

The **state diagram** corresponding to an FSM  $\mathcal{A}$  is a directed graph  $G = (Q, E)$  with edge labels  $(x, y) \in \Sigma \times \Delta$ . The edge set  $E$  is defined by

$$E \triangleq \{(q, \delta(q, x)) : q \in Q \text{ and } x \in \Sigma\}.$$

Each edge  $(q, \delta(q, x))$  is labeled  $(x, \lambda(q, x))$ .

The vertex  $q_0$  corresponding to the initial state of an FSM is usually marked in an FSM by a double circle.

We remark that a state diagram is in fact a **multi-graph**, namely, one allows more than one directed edge between two vertices.


Such edges are often called **parallel edges**. Note that the out-degree of every vertex in a state diagram equals  $|\Sigma|$ .

# Example: A two-state FSM

Consider the FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$  depicted in the next figure, where

$$Q = \{q_0, q_1\},$$

$$\Sigma = \Delta = \{0, 1\}.$$

 

Two tasks are often associated with synchronous circuits. These tasks are defined as follows.

- 1 Analysis: given a synchronous circuit  $C$ , describe its functionality by an FSM.
- 2 Synthesis: given an FSM  $\mathcal{A}$ , design a synchronous circuit  $C$  that implements  $\mathcal{A}$ .

The task of analyzing a synchronous circuit  $C$  is carried out as follows.

- 1 Define the FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$  as follows.
  - 1 The set of states is  $Q \triangleq \{0, 1\}^k$ , where  $k$  denotes the number of flip-flops in  $C$ .
  - 2 Define the initial state  $q_0$  to be the initial outputs of the flip-flops.
  - 3  $\Sigma = \{0, 1\}^\ell$ , where  $\ell$  denotes the number of input gates in  $C$ .
  - 4  $\Delta = \{0, 1\}^r$ , where  $r$  denotes the number of output gates in  $C$ .
  - 5 Define the transition function  $\delta : \{0, 1\}^k \times \{0, 1\}^\ell \rightarrow \{0, 1\}^k$  to be the function implemented by the combinational “part” of  $C$  for the inputs of the flip-flops.
  - 6 Define the output function  $\lambda : \{0, 1\}^k \times \{0, 1\}^\ell \rightarrow \{0, 1\}^r$  to be the function implemented by the combinational “part” of  $C$  for the output gates.

## Definition

A *counter*( $n$ ) is defined as follows.

**Inputs:** a clock CLK.

**Output:**  $N \in \{0, 1\}^n$ .

**Functionality:**

$$\forall t : \langle N_t \rangle = t(\text{mod } 2^n)$$

No input?! Input is “implied”: it is the (missing) reset signal!

# Counter Implementation


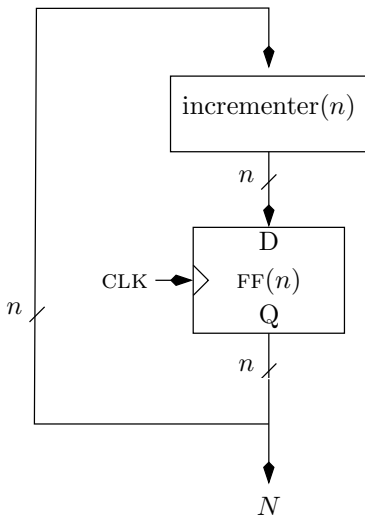


Figure: A synchronous circuit that implements a counter.

# Counter Analysis

 

**Figure:** An FSM of a counter(2). The output always equals binary representation of the state from which the edge emanates.



# A Counter with input

## Definition

A *counter*( $n$ ) is defined as follows.

**Inputs:**  $X \in \{0, 1\}$  and a clock CLK.


**Output:**  $N \in \{0, 1\}^n$ .

**Functionality:**


$$\forall t : \langle N_t \rangle = \sum_{i=0}^t X_i \pmod{2^n}$$

# Implementation of Counter with Input
 
# Analysis of Counter with Input for $n = 2$



# Sequential Adder: Analysis

 

**Figure:** an FSM of a sequential adder (each transition is labeled by a pair: the condition that the input satisfies and the value of the output).

# Revisiting Shift Registerers

Recall the definition of a shift register of  $n$  bits, that is:

**Inputs:**  $D[0](t)$  and a clock CLK.

**Output:**  $Q[n - 1](t)$ .

**Functionality:**  $Q[n - 1](t + n) = D[0](t)$ .

# Implementation of Shift Register


 


Figure: A 4-bit shift register.

# Analysis of Shift Register for $n = 2$

 

## Definition

A RAM( $2^n$ ) is specified as follows.

**Inputs:**  $Address[n - 1 : 0](t) \in \{0, 1\}^n$ ,  $D_{in}(t) \in \{0, 1\}$ ,  
 $R/\overline{W}(t) \in \{0, 1\}$  and a clock CLK.

**Output:**  $D_{out}(t) \in \{0, 1\}$ .

**Functionality** : The functionality of a RAM is specified by the following program:

- ① data: array  $M[2^n - 1 : 0]$  of bits.
- ② initialize:  $\forall i : M[i] \leftarrow 0$ .
- ③ For  $t = 0$  to  $\infty$  do
  - ①  $D_{out}(t) = M[\langle Address \rangle](t)$ .
  - ② For all  $i \neq \langle Address \rangle$ :  $M[i](t + 1) \leftarrow M[i](t)$ .
  - ③

$$M[\langle Address \rangle](t + 1) \leftarrow \begin{cases} D_{in}(t) & \text{if } R/\overline{W}(t) = 0 \\ M[\langle Address \rangle](t) & \text{else.} \end{cases}$$



 


Figure: A (partial) FSM of a RAM( $2^1$ ) (the “legend” of the edge labels:  $((D_{in}, \text{address}, R/\overline{W}), D_{out})$ ).

# Effect of Adding Initialization to a Synchronous Circuit

- $C$  is a synchronous circuit without an initialization signal (but we assume FFs output a specific value in  $t = 0$ ).
- Introduce an initialization signal *reset* that initializes the outputs of all flip-flops (namely, it cause the outputs of the flip-flops to equal a value that encodes the initial state).
- How? add a MUX after every FF that selects  $Q$  or initial-state based on *reset*.
- Denote the new synchronous circuit by  $\hat{C}$ .
- Let  $\mathcal{A}$  and  $\hat{\mathcal{A}}$  denote the FSMs that model the functionality of  $C$  and  $\hat{C}$ , respectively.
- What is the relation between  $\mathcal{A}$  and  $\hat{\mathcal{A}}$ ?

## Theorem

Let  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$  denote the FSM that models the functionality of the synchronous circuit  $C$ . Let

$\hat{\mathcal{A}} = \langle Q', \Sigma', \Delta', \delta', \lambda', q'_0 \rangle$  denote the FSM that models the synchronous circuit  $\hat{C}$ . Then,

$$Q' \triangleq Q,$$

$$q'_0 \triangleq q_0,$$

$$\Sigma' \triangleq \Sigma \times \{0, 1\},$$

$$\Delta' \triangleq \Delta,$$

$$\delta'(q, (\sigma, \text{reset})) \triangleq \begin{cases} \delta(q, \sigma), & \text{if } \text{reset} = 0, \\ \delta(q_0, \sigma), & \text{if } \text{reset} = 1, \end{cases}$$

$$\lambda'(q, (\sigma, \text{reset})) \triangleq \begin{cases} \lambda(q, \sigma), & \text{if } \text{reset} = 0, \\ \lambda(q_0, \sigma), & \text{if } \text{reset} = 1. \end{cases}$$

# Synthesis: FSM $\mapsto$ Sync Circuit

Given an FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ , the task of designing a synchronous circuit  $C$  that implements  $\mathcal{A}$  is carried out as follows.

- 1 Encode  $Q, \Sigma$  and  $\Delta$  by binary strings. Formally, let  $f, g, h$  denote one-to-one functions, where

$$f : Q \rightarrow \{0, 1\}^k$$

$$g : \Sigma \rightarrow \{0, 1\}^\ell$$

$$h : \Delta \rightarrow \{0, 1\}^r.$$

- 2 Design a combinational circuit  $C_\delta$  that implements the (partial) Boolean function  $B_\delta : \{0, 1\}^k \times \{0, 1\}^\ell \rightarrow \{0, 1\}^k$  defined by

$$B_\delta(f(x), g(y)) \triangleq f(\delta(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

- 3 Design a combinational circuit  $C_\lambda$  that implements the (partial) Boolean function  $B_\lambda : \{0, 1\}^k \times \{0, 1\}^\ell \rightarrow \{0, 1\}^r$

$$B_\lambda(f(x), g(y)) \triangleq h(\lambda(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

- How many flip-flops are required?  $f : Q \rightarrow \{0,1\}^k$  is one-to-one. So

$$k \geq \log_2 |Q|$$

- It is not clear that minimizing  $k$  is always a good idea. Certain encodings lead to more complicated Boolean functions  $B_\delta$  and  $B_\lambda$ .
- The question of selecting a “good” encoding is a very complicated task, and there is no simple solution to this problem.

## Example: A two-state FSM

Consider the FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$  depicted in the next figure, where

$$Q = \{q_0, q_1\},$$

$$\Sigma = \Delta = \{0, 1\}.$$

 


Figure: A two-state FSM.

## Two-State FSMs: Synthesis

Given an FSM  $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ , the synchronous circuit  $C$  that is obtained by executing the synthesis procedure is as follows. We encode  $Q, \Sigma$  and  $\Delta$  by binary strings. Formally, let  $f, g, h$  denote one-to-one functions, where

$$f : Q \rightarrow \{0, 1\}$$

$$g : \Sigma \rightarrow \Sigma$$

$$h : \Delta \rightarrow \Delta,$$

where

$$f(q_0) = 0, f(q_1) = 1,$$

and

$$\forall x \in \{0, 1\} : g(x) = h(x) = x.$$

We design a combinational circuit  $C_\delta$  that implements the Boolean function  $B_\delta : \{0, 1\}^2 \rightarrow \{0, 1\}$  defined by

$$B_\delta(f(x), g(y)) \triangleq f(\delta(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

$f(x)$	$g(y)$	$f(\delta(x, y))$
0	0	1
1	0	1
0	1	0
1	1	0

**Table:** The truth table of  $B_\delta$ .

It follows that  $B_\delta(f(x), g(y)) = \text{NOT}(g(y))$ .



We design a combinational circuit  $C_\lambda$  that implements the Boolean function  $B_\lambda : \{0, 1\}^2 \rightarrow \{0, 1\}$  defined by

$$B_\lambda(f(x), g(y)) \triangleq h(\lambda(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

$f(x)$	$g(y)$	$h(\lambda(x, y))$
0	0	1
1	0	1
0	1	0
1	1	1

**Table:** The truth table of  $B_\lambda$ .

It follows that  $B_\lambda(f(x), g(y)) = f(x) \vee \overline{g(y)}$ .

# Two-State FSMs: Synthesis - the Synch. circuit $C$

The synchronous circuit in canonic form constructed from a flip-flops and two combinational circuits is depicted in Figure ??.

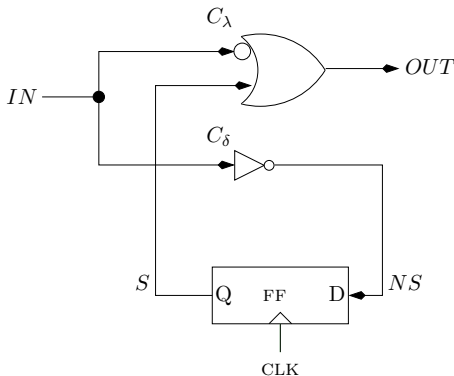


Figure: Synthesis of  $\mathcal{A}$ .

# Summary of Part 2

- Definition of synchronous circuits.
- Simulation algorithm.
- Synchronous circuits in canonic form.
- Initialization & *reset* signal.
- Functionality: finite-state machines & state diagrams.
- Analysis and synthesis of synchronous circuits.
- FSM's are not a useful model for synchronous circuit with many FF's because  $|States| = 2^{|FF's|}$ .