

Digital Logic Design: a rigorous approach ©

Chapter 14: Selectors

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

May 14, 2020

Book Homepage:

<http://www.eng.tau.ac.il/~guy/Even-Medina>

Multiplexer (MUX)

Definition

A MUX-gate is a combinational gate that has three inputs $D[0]$, $D[1]$, S and one output Y . The functionality is defined by

$$Y = \begin{cases} D[0] & \text{if } S = 0 \\ D[1] & \text{if } S = 1. \end{cases}$$

Note that we could have used the shorter expression $Y = D[S]$ to define the functionality of a MUX-gate.

Definition

An $(n:1)$ -MUX is a combinational circuit defined as follows:

Input: **data input** $D[n-1:0]$ and **select input** $S[k-1:0]$
where $k = \lceil \log_2 n \rceil$.

Output: $Y \in \{0,1\}$.

Functionality:

$$Y = D[\langle \vec{S} \rangle].$$

To simplify the discussion, we will assume in this chapter that n is a power of 2, namely, $n = 2^k$.


Example

Let $n = 4$ and $D[3:0] = 0101$. If $S[1:0] = 00$, then $Y = D[0] = 1$. If $S[1:0] = 01$, then $Y = D[1] = 0$.

We describe two implementations of $(n:1)$ -MUX.

- translate the number $\langle \vec{S} \rangle$ to 1-out-of- n representation (using a decoder).
- tree based.


decoder based $(n:1)$ -MUX

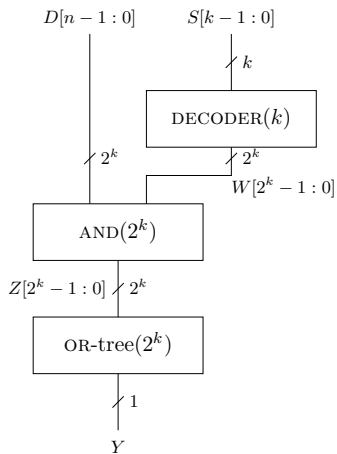

Claim

The $(n:1)$ -MUX design is correct.


decoder based $(n:1)$ -MUX - cost

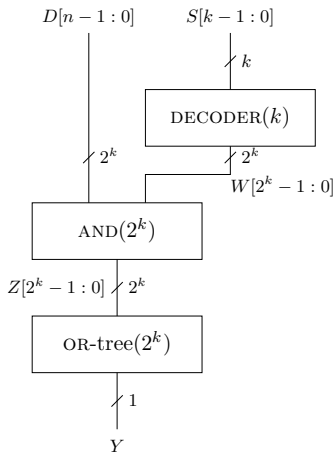

Claim

The cost of the $(n:1)$ -MUX design is $\Theta(n)$.

decoder based $(n:1)$ -MUX - delay

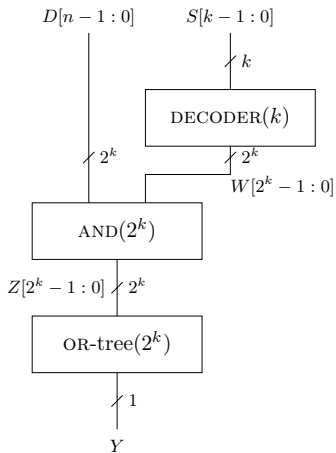

Claim

The delay of the $(n:1)$ -MUX design is $\Theta(\log n)$.

$(n:1)$ -MUX - lower bounds

Claim

The cone of the Boolean function implemented by a $(n:1)$ -MUX circuit contains at least n elements.

Consider combinational circuits with gates of constant fan-in.


Corollary

The cost of the $(n:1)$ -MUX design is asymptotically optimal.

Corollary

The delay of the $(n:1)$ -MUX design is asymptotically optimal.


tree based $(n:1)$ -MUX

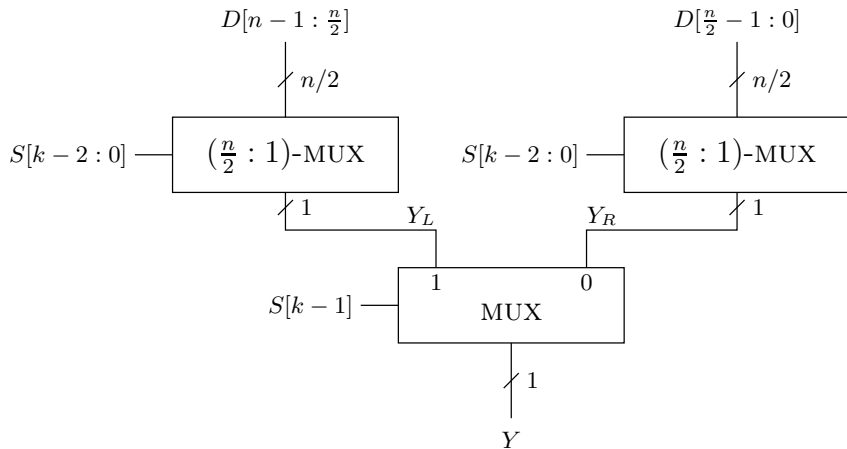

Claim

The $(n:1)$ -MUX design is correct.


tree based $(n:1)$ -MUX - cost

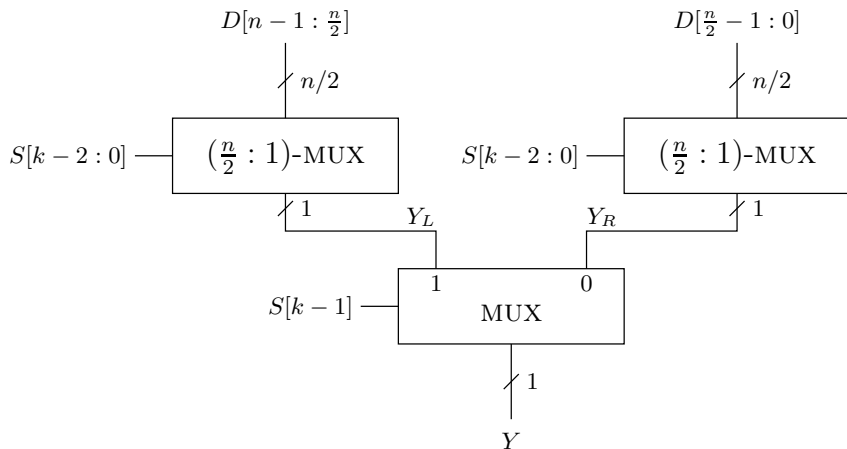

Claim

The cost of the $(n:1)$ -MUX design is $\Theta(n)$.

tree based $(n:1)$ -MUX - delay

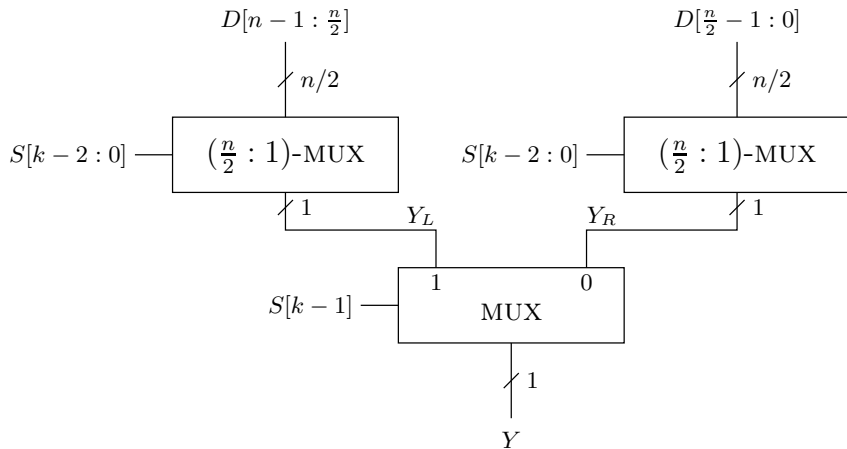

Claim

The delay of the $(n:1)$ -MUX design is $\Theta(\log n)$.

- Both implementations are asymptotically optimal with respect to cost and delay.
- The cost/delay table suggests that the tree-like implementation is cheaper and faster.
- Fast and cheap implementations of MUX-gates in CMOS technology (called “pass transistors”) do not restore the signals well. This means that long paths consisting only of such MUX-gates are not allowed (must interleave with invertors to restore the signals).
- What about physical layout? Which design has a smaller “drawing”? (beyond the scope of this course)
- Conclusion: our simplified model cannot be used to deduce conclusively which multiplexer design is better.